

MSC 1012 questions for Chapter 8 set 4

Resistance:

NAME _____

- 1) A device draws 12.5 A when driven with a 110 V supply. What is the resistance of the device?

ANS _____

- 2) What is the current and resistance of a 28 W light bulb operating off of 120 V?

ANS _____

ANS _____